

EE 464 Homework 3

Burak Kemal Kara

April 22, 2020

1 Derivation of Input to Output TF

To derive TF, first I will find small signal circuit equivalent. Forward converter can be treated as a buck converter with $V_{in} = n \cdot V_{in}$ where n is transformer ratio.

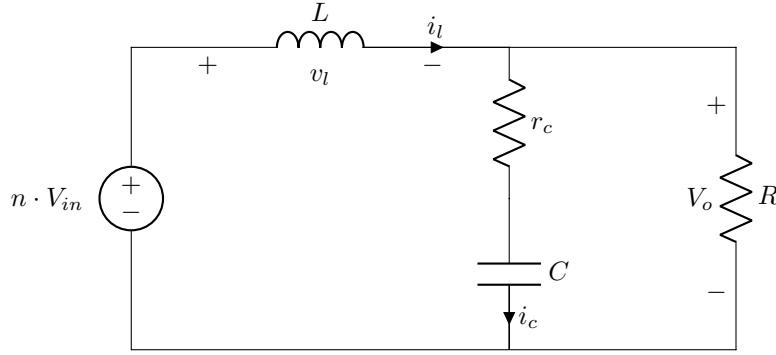


Figure 1: Simplified Forward Converter when switch is on

KVL at the outer path,

$$-nV_{in} + L \frac{di}{dt} + i_o R = 0 \quad (1)$$

Since,

$$i_o = i_l - i_c \quad (2)$$

$$L \frac{di}{dt} = nV_{in} - Ri_l + Ri_c \quad (3)$$

Find i_c by KVL on inductor and capacitor

$$-nV_{in} + L \frac{di}{dt} + i_c r_c + V_c = 0 \quad (4)$$

$$i_c = \frac{nV_{in} - L \frac{di}{dt} - V_c}{r_c} \quad (5)$$

Insert i_c into equation 3,

$$\hat{i}_l = \frac{di}{dt} = \frac{nV_{in}}{L} - \frac{r_c R}{(r_c + R)L} \frac{R}{(r_c + R)L} V_c \quad (6)$$

We know that $R \gg r_c$ so we can simplify equation as,

$$\hat{i}_l = \frac{nV_{in}}{L} - \frac{r_c}{L} i_l - \frac{1}{L} v_c \quad (7)$$

Start derive V_c by KCL at output node,

$$i_c = i_l - \frac{V_o}{R} \quad (8)$$

Since,

$$v_o = v_c + r_c i_c \quad (9)$$

$$i_c = \frac{R}{R + r_c} i_l - \frac{1}{R + r_c} v_l \quad (10)$$

Since,

$$\hat{v}_c = \frac{i_c}{C} \quad (11)$$

$$\hat{v}_c = \frac{R}{C(R + r_c)} i_l - \frac{1}{C(R + r_c)} v_l \quad (12)$$

We know that $R \gg r_c$ so we can simplify equation as,

$$\hat{V}_c = \frac{1}{C} i_l - \frac{1}{RC} v_l \quad (13)$$

According to state space equations,

$$\begin{bmatrix} \hat{i}_l \\ \hat{v}_c \end{bmatrix} = \begin{bmatrix} -\frac{r_c}{L} & -\frac{1}{RC} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_l \\ v_c \end{bmatrix} + \begin{bmatrix} \frac{n}{L} \\ 0 \end{bmatrix} V_{in} \quad (14)$$

For switch off position A matrix hasn't changed. But B matrix multiplied with duty ratio so,

$$\begin{bmatrix} \hat{i}_l \\ \hat{v}_c \end{bmatrix} = \begin{bmatrix} -\frac{r_c}{L} & -\frac{1}{RC} \\ \frac{1}{C} & -\frac{1}{RC} \end{bmatrix} \begin{bmatrix} i_l \\ v_c \end{bmatrix} + \begin{bmatrix} \frac{dn}{L} \\ 0 \end{bmatrix} V_{in} \quad (15)$$

Find v_o as state space variables,

$$v_o = Ri_o = R(i_l - i_c) = R(i_l - (\frac{v_o - v_c}{r_c})) \quad (16)$$

$$v_o = \frac{r_c R}{r_c + 1} i_l + \frac{1}{(r_c + 1)} v_c \quad (17)$$

Since $r_c \ll 1$,

$$v_o = r_c R i_l + v_c \quad (18)$$

$$C = \begin{bmatrix} Rr_c \\ 1 \end{bmatrix} \quad (19)$$

$$\frac{v_o(s)}{d(s)} = C^T [SI - A]^{-1} B V_{in} \quad (20)$$

After a lengthy evaluation control to output TF is,

$$G_{vd} = \left. \frac{\tilde{v}_o}{\tilde{d}} \right|_{\tilde{v}_i=0} = \frac{nV_{in}}{RLC} \left[\frac{sR^2Cr_c + R + 1}{s^2 + s(\frac{r_c}{L} + \frac{1}{RC}) + \frac{1}{LC}} \right] \quad (21)$$